

Lecture-1

Mid - 1, 2, 5, 6

Topics

Final - 2, 3, 4

- 1] Transformer
 - 2] Induction Motor
 - 3] Synchronous generator
 - 4] Synchronous Motor
 - 5] DC Generator
 - 6] DC Motor
- } DC machines.

$$Z = R + jX \rightarrow \text{[Short circuit]}$$

$$\text{for } L=0, Z \approx 0 \text{ [DC]}$$

$$\text{for } C=0, Z \approx \infty \text{ [DC]}$$

↓
[open circuit]

Transformer

a transformer is a static electrical device that transfers electrical power from one circuit to another circuit through electromagnetic induction.

$$V_{\text{emf}} = N \frac{d\phi}{dt}$$

N = Number of turns

ϕ = Magnetic flux

$\frac{d\phi}{dt}$ = Rate of change of flux


Turn Ratio

$$a = \frac{N_p}{N_s}$$

N_p = Number of primary turns

N_s = " " secondary
"

Ideal Transformer [$P_{pri} = P_{sec}$]

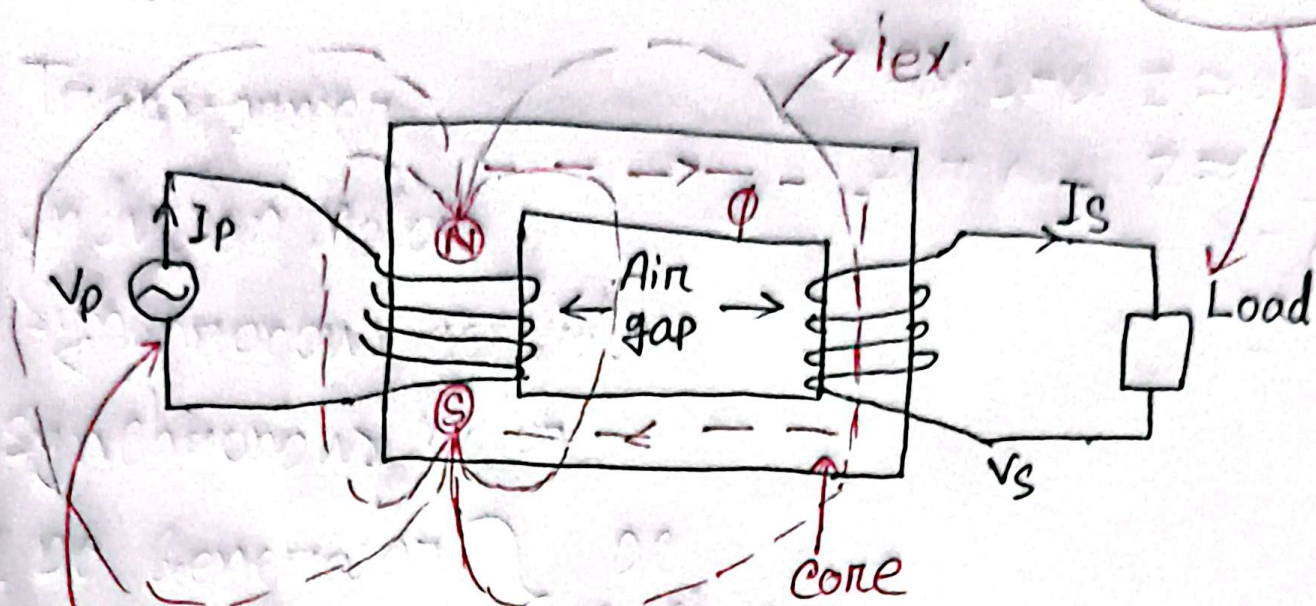

Primary Side

$$X_L = 2\pi f L = 0$$

$$X_C = \frac{1}{2\pi f C} = \infty$$

secondary side

$$N \uparrow \quad V \uparrow \quad I \downarrow \Rightarrow \frac{N_p}{N_s} = \frac{V_p}{V_s} = \frac{I_s}{I_p}$$

Case-1 [$a > 1$]

$$a \uparrow \quad \frac{N_p}{N_s} \uparrow$$

$$\begin{aligned} N_p &> N_s \\ V_p &> V_s \\ I_p &< I_s \end{aligned}$$

Step Down

Case-2 [$a < 1$]

$$a \downarrow \quad \frac{N_p}{N_s} \downarrow$$

$$\begin{aligned} N_p &< N_s \\ V_p &< V_s \\ I_p &> I_s \end{aligned}$$

Step UP

Case-3

$$a = 1$$