

Summer 2025

ENERGY CONVERSION-I

EEE 221

LECTURE-03

TR


Transformers



Inspiring Excellence

Chapter 2 Transformers

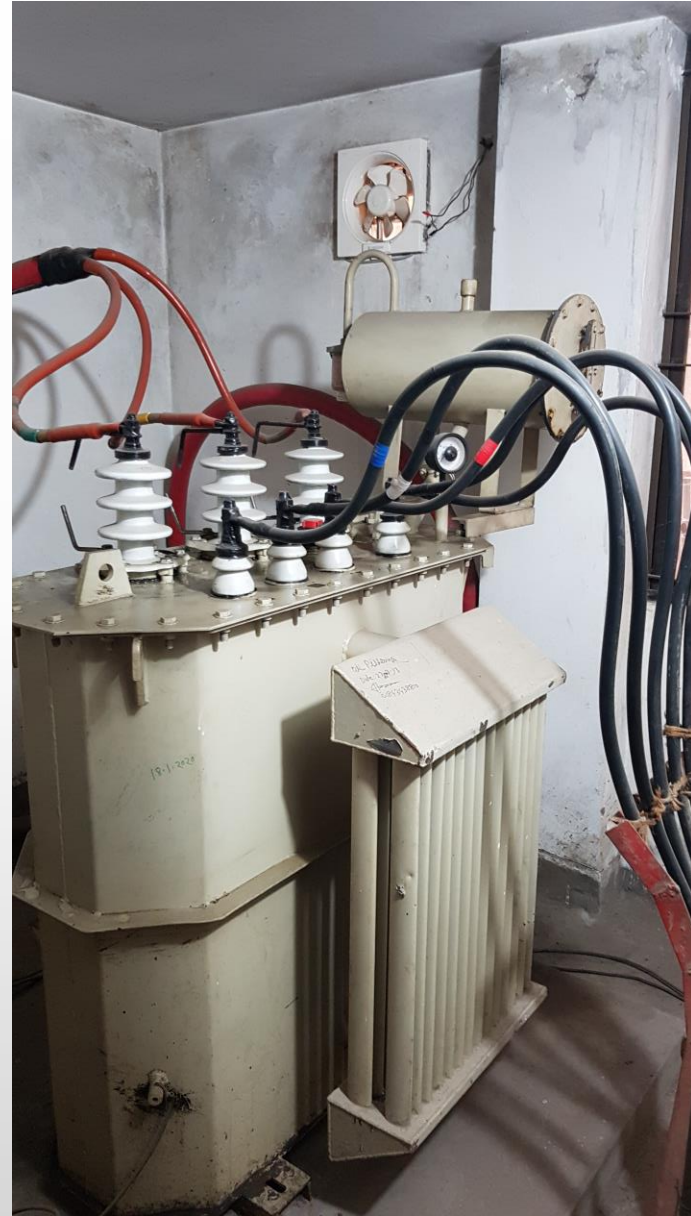- Types and construction of transformers
- The ideal transformer
- Theory of operation of real single-phase transformers
- **Equivalent circuit of a transformer**
- **Transformer voltage regulation and efficiency**
- Transformer taps and voltage regulation
- The autotransformer
- Three-phase transformer
- Instrument transformers



Measure the equivalent circuit parameters

- There are two types of measurements used for determination the equivalent circuit parameters
- ***Open circuit test*** – used to measure excitation branch
- ***Short circuit test*** – used to measure series branch

Open circuit test

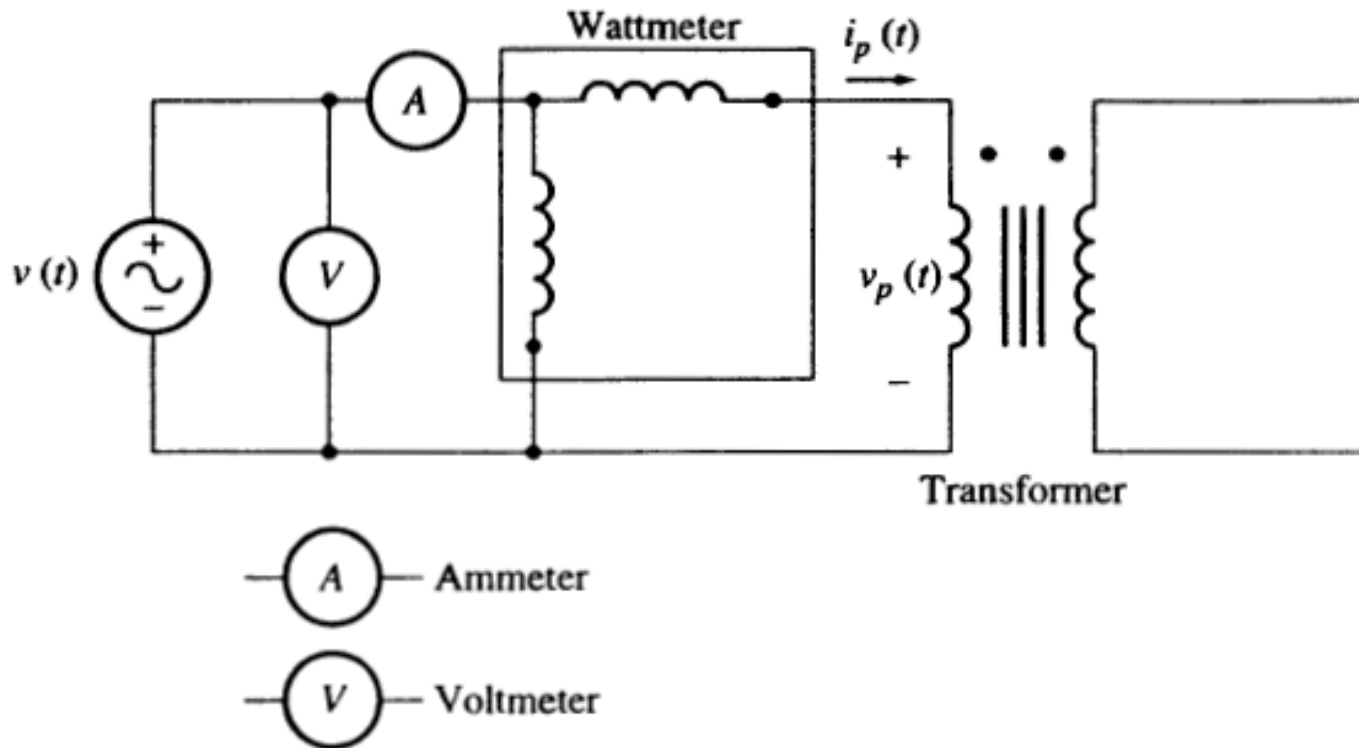


Figure 2-19

Open circuit test / Page-90

- Under the open circuit condition, all the input current flows through the excitation branch (Since the current is small, the test usually performs at high voltage side)

$$G_C = \frac{1}{R_C} \quad (2-40)$$

$$B_M = \frac{1}{X_M} \quad (2-41)$$

$$\begin{aligned} Y_E &= G_C - jB_M \\ &= \frac{1}{R_C} - j\frac{1}{X_M} \end{aligned} \quad (2-43)$$

$$|Y_E| = \frac{I_{OC}}{V_{OC}} \quad (2-44)$$

$$\text{PF} = \cos \theta = \frac{P_{OC}}{V_{OC} I_{OC}} \quad (2-45)$$

$$\theta = \cos^{-1} \frac{P_{OC}}{V_{OC} I_{OC}} \quad (2-46)$$

$$\begin{aligned} Y_E &= \frac{I_{OC}}{V_{OC}} \angle -\theta \\ &= \frac{I_{OC}}{V_{OC}} \angle -\cos^{-1} \text{PF} \end{aligned} \quad (2-47)$$

Short circuit test

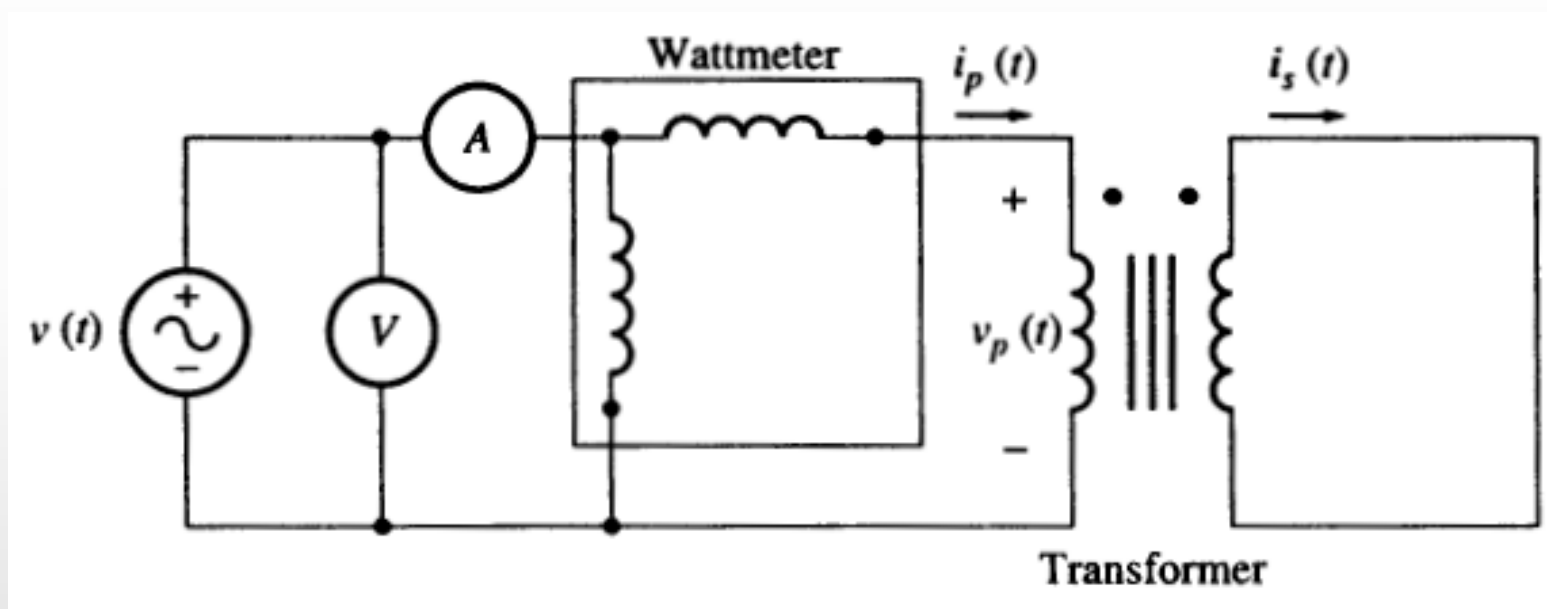


Figure 2-20

Short circuit test

- At secondary side short circuit condition, the input voltage must be a very low value to prevent input large short circuit current (usually performs at low voltage side)

$$|Z_{SE}| = \frac{V_{SC}}{I_{SC}} \quad (2-48)$$

$$PF = \cos \theta = \frac{P_{SC}}{V_{SC} I_{SC}} \quad (2-49)$$

$$\theta = \cos^{-1} \frac{P_{SC}}{V_{SC} I_{SC}} \quad (2-50)$$

$$Z_{SE} = \frac{V_{SC} \angle 0^\circ}{I_{SC} \angle -\theta^\circ} = \frac{V_{SC}}{I_{SC}} \angle \theta^\circ \quad (2-51)$$

$$\begin{aligned} Z_{SE} &= R_{eq} + jX_{eq} \\ &= (R_P + a^2 R_S) + j(X_P + a^2 X_S) \end{aligned} \quad (2-52)$$

Open and Short circuit Test Summary

- Open Circuit Test (**Core loss**)

H.V side open

Measured in L.V side

Components **R_c** and **X_m** (Ref. to low volt.)

- Short Circuit Test (**Cu loss**)

L.V side Short Ckt. (Rated current flow)

Measured in H.V side (for low current)

Series Elements **R_{eq}** & **X_{eq}** (Ref. to High volt)

- In the math for final equivalent circuit, all the elements must be referred to the same side.

Example 2–2. The equivalent circuit impedances of a 20-kVA, 8000/240 V, 60-Hz transformer are to be determined. The open-circuit test was performed on the secondary side of the transformer (to reduce the maximum voltage to be measured) and the short-circuit test were performed on the primary side of the transformer (to reduce the maximum current to be measured). The following data were taken:

Open-circuit test (on secondary)	Short-circuit test (on primary)
$V_{OC} = 240 \text{ V}$	$V_{SC} = 489 \text{ V}$
$I_{OC} = 7.133 \text{ A}$	$I_{SC} = 2.5 \text{ A}$
$P_{OC} = 400 \text{ W}$	$P_{SC} = 240 \text{ W}$

Find the impedances of the approximate equivalent circuit referred to the primary side, and sketch that circuit.

Solution

The turns ratio of this transformer is $a = 8000/240 = 33.3333$. The power factor during the *open-circuit* test is

$$PF = \cos \theta = \frac{P_{OC}}{V_{OC} I_{OC}} \quad (2-45)$$



Inspiring Excellence

Solution:

$$PF = \cos \theta = \frac{P_{oc}}{V_{oc} I_{oc}}$$

$$\cos \theta = \frac{400 W}{(240 V)(7.133 A)}$$

$$\cos \theta = 0.234 \text{ Lagging}$$

$$\begin{aligned}\therefore \theta &= \cos^{-1}(0.234) \\ &= 76.5^\circ\end{aligned}$$

The excitation admittance is given by :

$$Y_E = \frac{I_{oc}}{V_{oc}} \angle -\theta$$

$$= \frac{I_{oc}}{V_{oc}} \angle -76.5^\circ$$

$$= \frac{7.133 A}{240 V} \angle -76.5^\circ$$

$$= 0.0297 \angle -76.5^\circ S$$

$$\therefore Y_E = 0.00693 - j0.02888$$

$$= \frac{1}{R_e} - j \frac{1}{X_M}$$

Therefore, the values of the excitation branch *referred to the low-voltage (secondary) side* are

$$R_C = \frac{1}{0.00693} = 144 \, \Omega$$

$$X_M = \frac{1}{0.02888} = 34.63 \, \Omega$$

The power factor during the *short-circuit* test is

$$\text{PF} = \cos \theta = \frac{P_{sc}}{V_{sc} I_{sc}} \quad (2-49)$$

$$\text{PF} = \cos \theta = \frac{240 \, \text{W}}{(489 \, \text{V})(2.5 \, \text{A})} = 0.196 \text{ lagging}$$

$$\begin{aligned} \therefore \theta &= \cos^{-1}(0.196) \\ &= 78.7^\circ \end{aligned}$$

\therefore The series impedance is given by;

$$Z_{SE} = \frac{V_{sc}}{I_{sc}} \angle \theta$$

$$= \frac{489 \, \text{V}}{2.5 \, \text{A}} \angle 78.7^\circ$$

$$= 195.6 \angle 78.7^\circ = 38.4 + j192 \, \Omega$$

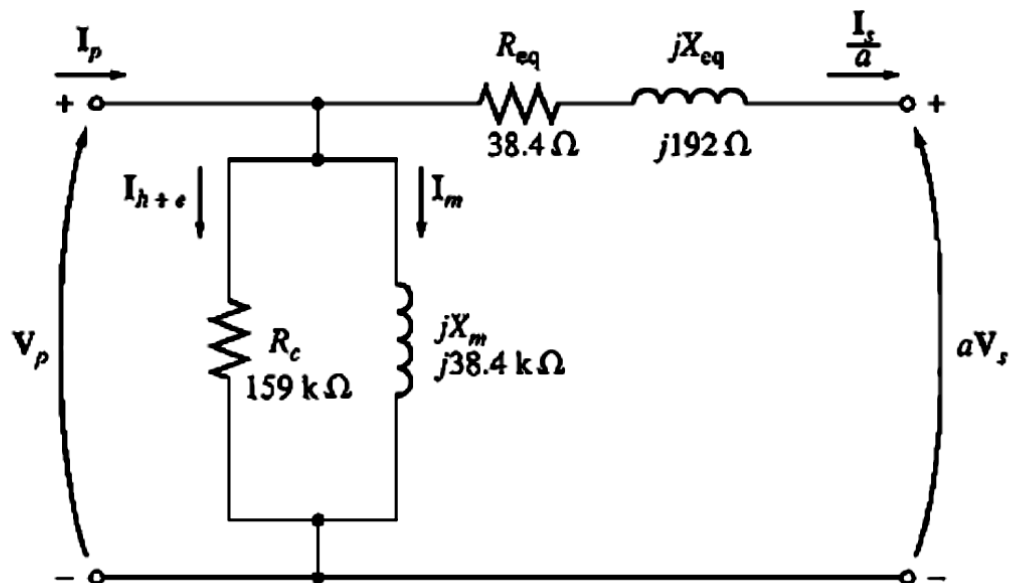


FIGURE 2-21

The equivalent circuit of Example 2-2.

Therefore, the equivalent resistance and reactance *referred to the high-voltage (primary) side* are

$$R_{eq} = 38.4 \, \Omega \quad X_{eq} = 192 \, \Omega$$

The resulting simplified equivalent circuit referred to the high-voltage (primary) side can be found by converting the excitation branch values to the high-voltage side.

$$R_{C,P} = a^2 R_{C,S} = (33.333)^2 (144 \, \Omega) = 159 \, k\Omega$$

$$X_{M,P} = a^2 X_{M,S} = (33.333)^2 (34.63 \, \Omega) = 38.4 \, k\Omega$$

The resulting equivalent circuit is shown in Figure 2-21.

Transformer voltage regulation and efficiency

Because a real transformer has series impedances within it, the output voltage of a transformer varies with the load even if the input voltage remains constant. To conveniently compare transformers in this respect, it is customary to define a quantity called *voltage regulation* (VR). *Full-load voltage regulation* is a quantity that compares the output voltage of the transformer at no load with the output voltage at full load. It is defined by the equation

$$\text{VR} = \frac{V_{S, \text{nl}} - V_{S, \text{fl}}}{V_{S, \text{fl}}} \times 100\% \quad (2-61)$$

Since at no load, $V_S = V_P / a$, the voltage regulation can also be expressed as

$$\text{VR} = \frac{V_P / a - V_{S, \text{fl}}}{V_{S, \text{fl}}} \times 100\% \quad (2-62)$$